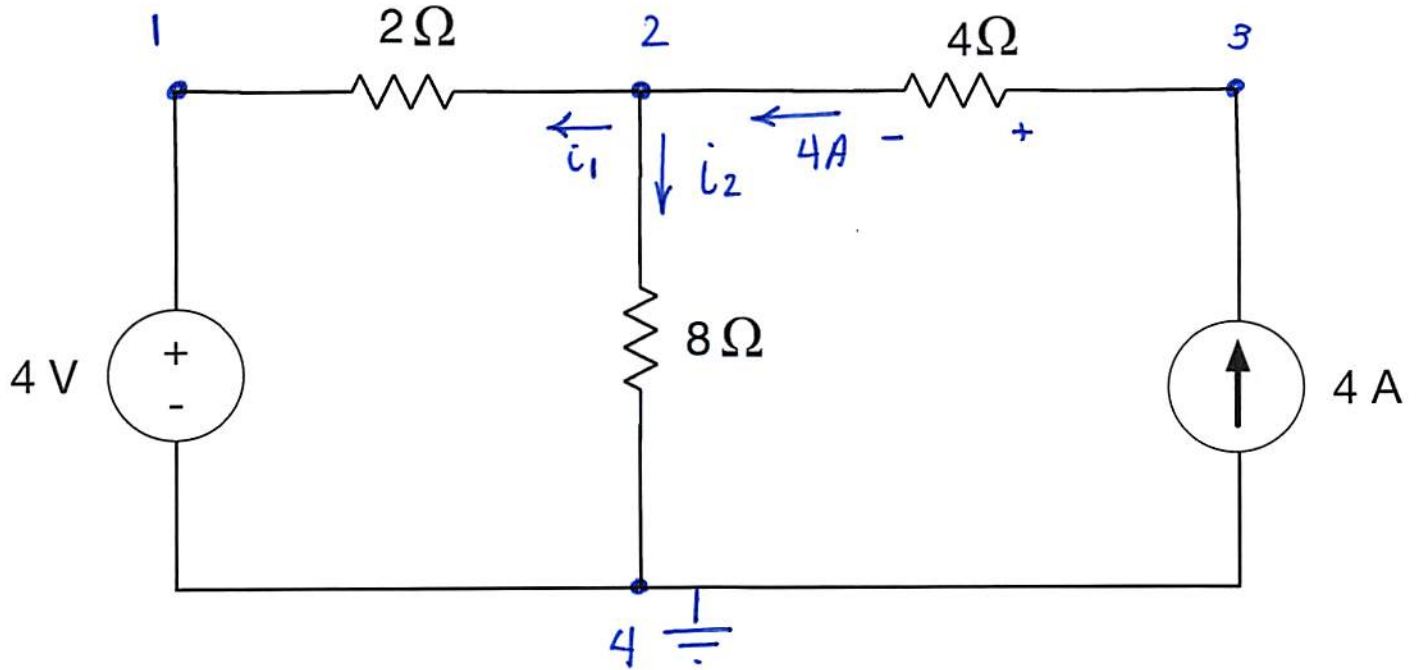




1 - Find the voltages at all the nodes.



$$V_4 = 0V$$

$$\text{kcl @ 2} \quad i_1 + i_2 = 4$$

$$V_1 = 4V$$

$$\Rightarrow \frac{V_2 - 4}{2} + \frac{V_2}{8} = 4$$

$$\Rightarrow V_2 = 9.6V$$


Alternate approach

$$\frac{V_3 - V_2}{4} = 4 \Rightarrow$$

$$V_3 = 4 \times 4 + V_2 = 25.6V$$

$$\left. \begin{aligned} V_3 &= V_2 + \text{Voltage drop across} \\ &\quad \text{the } 4\Omega \text{ resistor} \\ &= V_2 + 4 \times 4 = 25.6V \end{aligned} \right\}$$

2 - Find v_1 , v_2 , and v_3

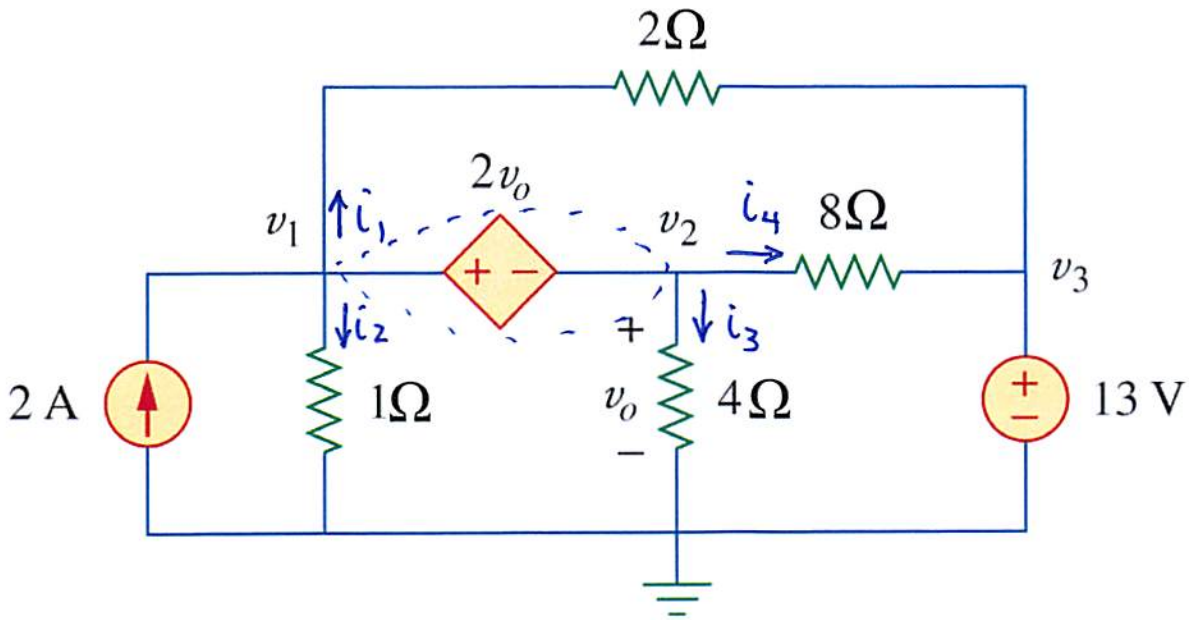

KCL @ SN $2 = i_1 + i_2 + i_4 + i_3$

$$2 = \frac{v_1 - 13}{2} + \frac{v_1}{1} + \frac{v_2}{4} + \frac{v_2 - 13}{8} \quad (2)$$

at the super node

$$v_2 + 2v_0 = v_1$$



$$v_2 + 2v_2 = v_1$$

$$3v_2 = v_1 \quad (1)$$

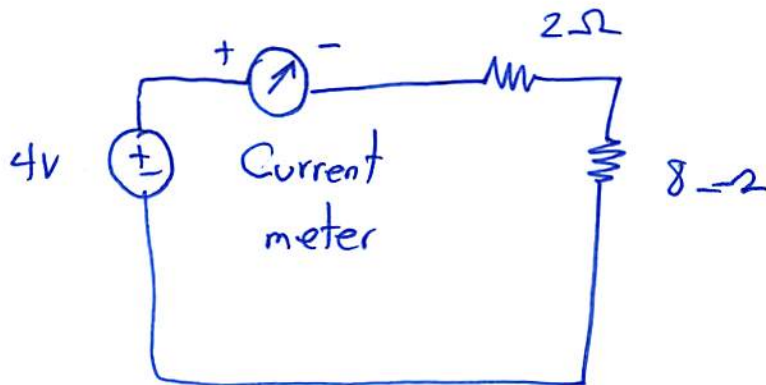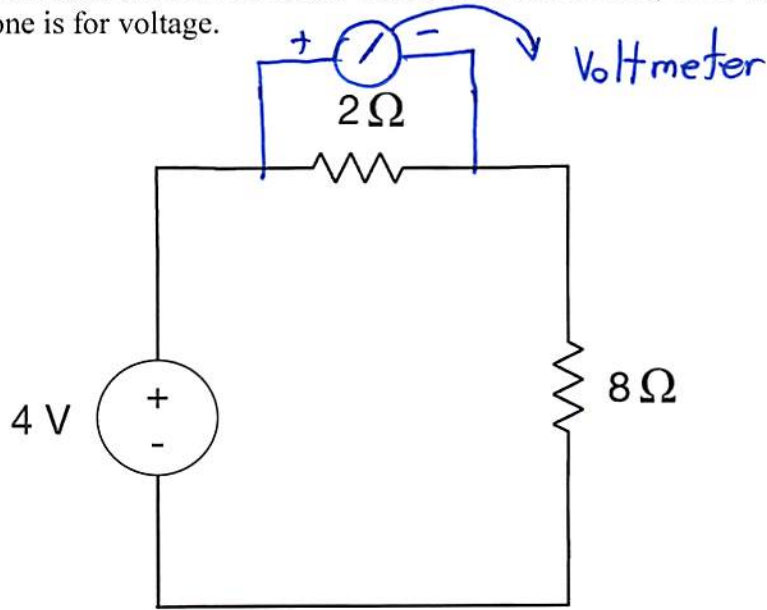
(1), (2) solved gives

$$v_1 = \frac{243}{39} \text{ V} \quad v_2 = \frac{81}{39} \text{ V} \quad v_3 = 13 \text{ V}$$

3 – How do you connect a voltmeter and current meter to measure the voltage across and the current through the 2 ohm resistor, respectively? Make sure you draw a very clear diagram and show where the terminals of the voltmeter and current meter will be connected. Also, label which diagram is for measuring current and which one is for voltage.



4 – Find current I in the circuit

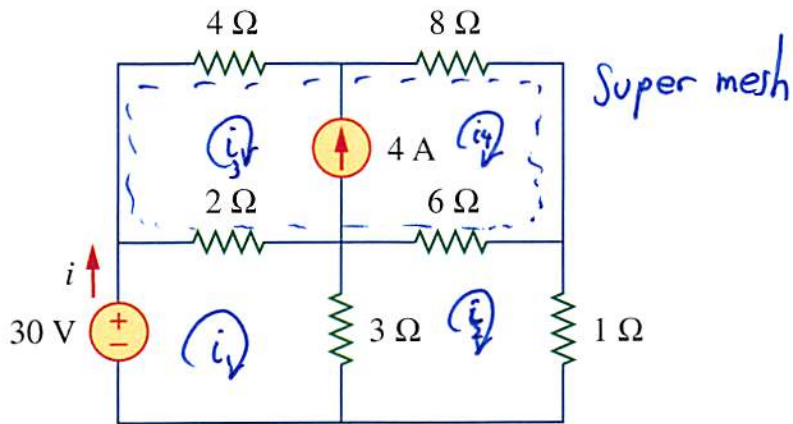

$$\text{Super mesh: } 2(i_3 - i_1) + 4i_3 + 8i_4 + 6(i_4 - i_2) = 0$$

$$\text{mesh 1: } 2(i_1 - i_3) + 3(i_1 - i_2) - 30 = 0$$

$$\text{mesh 2: } 3(i_2 - i_1) + 6(i_2 - i_4) + i_2 = 0$$

$$\text{Super mesh: } 6i_3 + 14i_4 - 2i_1 - 6i_2 = 0$$


$$\text{mesh 1: } 5i_1 - 3i_2 - 2i_3 = 30$$

$$\text{mesh 2: } 10i_2 - 3i_1 - 6i_4 = 0$$

$$\text{KCL: } i_4 - i_3 = 4$$

$$\text{Solving for } i_1 = 8.561 \text{ A}$$

5. Use nodal analysis to find v_0

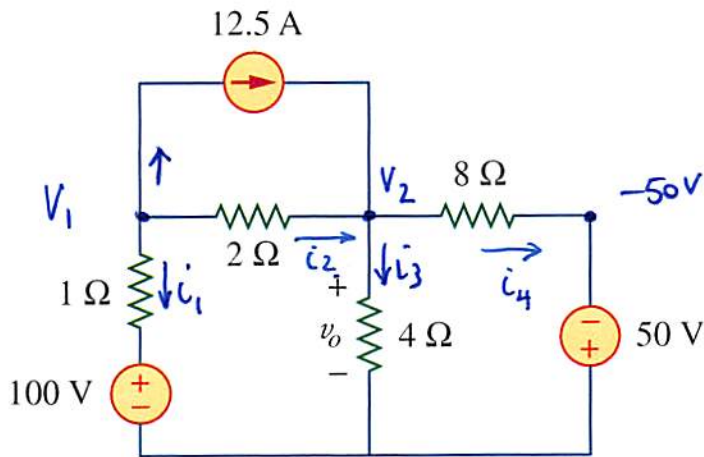

Node 1: $i_1 + i_2 + 12.5 = 0$

$$\frac{V_1 - 100}{1} + \frac{V_1 - V_2}{2} + 12.5 = 0 \Rightarrow \boxed{3V_1 - V_2 = 175}$$

Node 2: $i_2 + 12.5 = i_3 + i_4$

$$\frac{V_1 - V_2}{2} + 12.5 = \frac{V_2}{4} + \frac{V_2 + 50}{8}$$

$$\boxed{4V_1 - 7V_2 = -50}$$

$$V_1 = 47V$$

$$\boxed{V_2 = 34V = v_0}$$