


Boise State University
Electrical Engineering Department

EE 210: Circuits I
Spring 2017


Due Date:

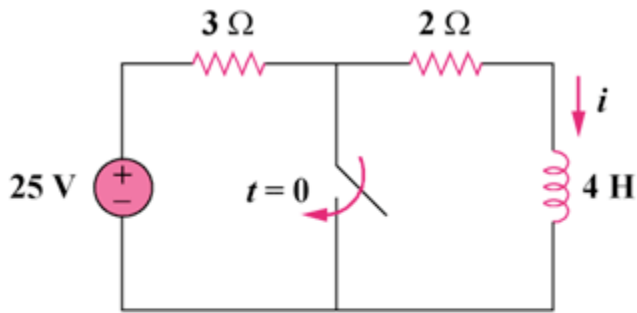Problem 1.

Determine the inductor current $i(t)$ for both $t < 0$ and $t > 0$ for each of the circuits in Fig. below.



(a)

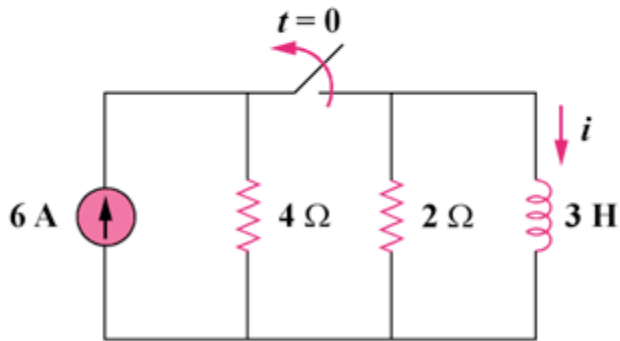

(b)

Problem 2.

Find $i_1(t)$ and $i_2(t)$ for $t > 0$ in the circuit of Fig. below.

