


Boise State University
Electrical Engineering Department

EE 210: Circuits I
Spring 2018

Due Date: Wed. 3/07/2018


Problem 1

Use superposition to find v_o in the circuit.

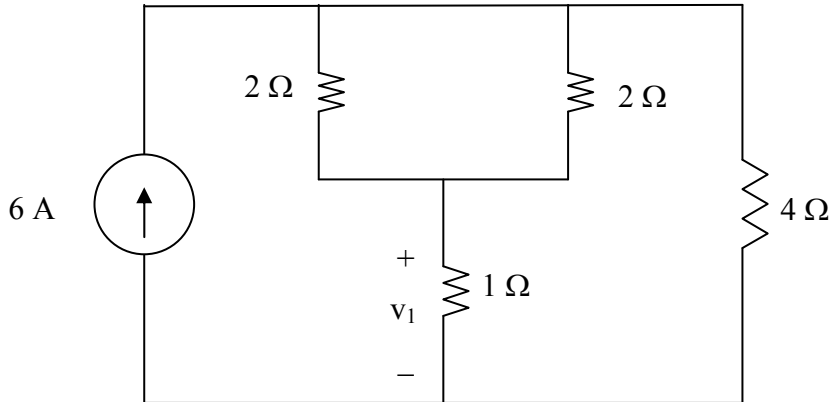


Problem 2

Use superposition to find v_o in the circuit.

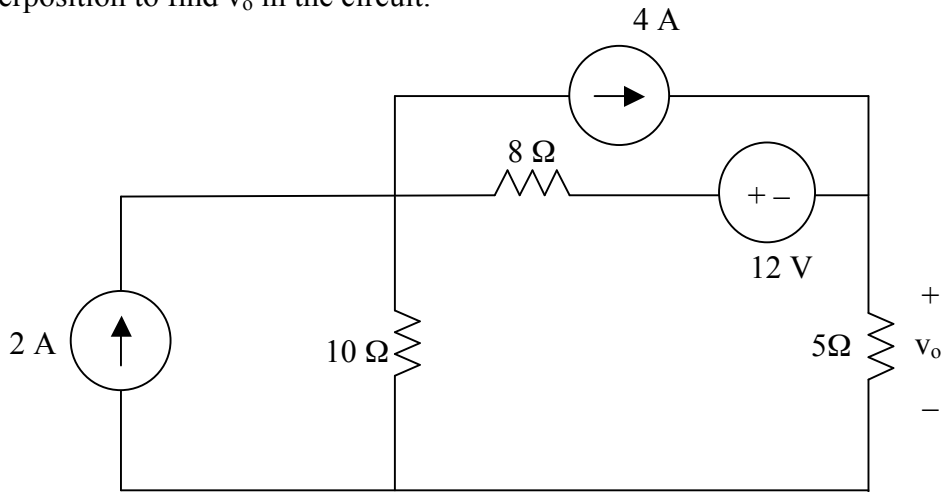

Problem 3

Use superposition to solve for v_x in the circuit

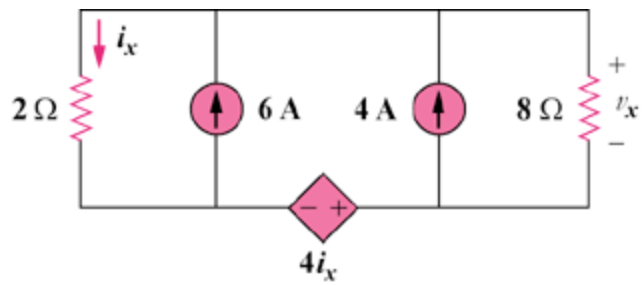

Problem 4

Use superposition to obtain v_x in the circuit. Check your result using *PSpice*.

