

Boise State University
Electrical Engineering Department

EE 210: Circuits I
Spring 2017


Due Date: Wed. 3/15/2017

Problem 1.

If the voltage across a 5-F capacitor is $2te^{-3t}$ V, find the current and the power.

Problem 2.

The voltage across a 4- μ F capacitor is shown. Find the current waveform.

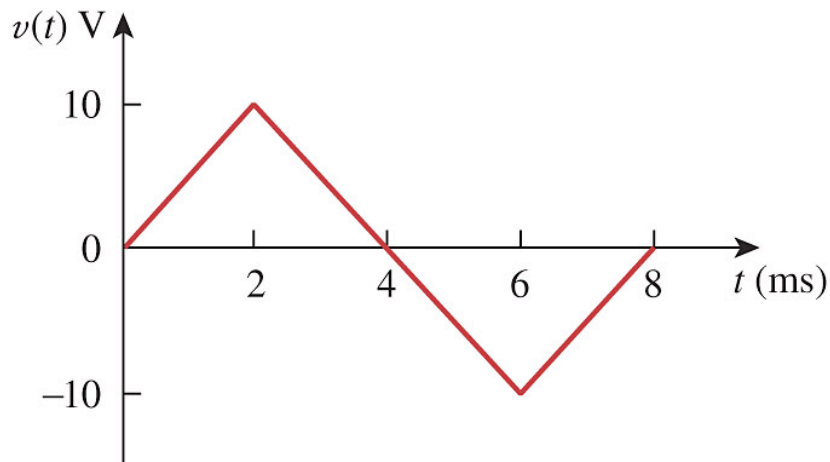


Problem 3.

At $t=0$, the voltage across a 50-mF capacitor is 10 V. Calculate the voltage across the capacitor for $t > 0$ when current $4t$ mA flows through it.


Problem 4

A 4-mF capacitor has the current waveform shown in Fig. 6.48. Assuming that $v(0)=10\text{V}$, sketch the voltage waveform $v(t)$.

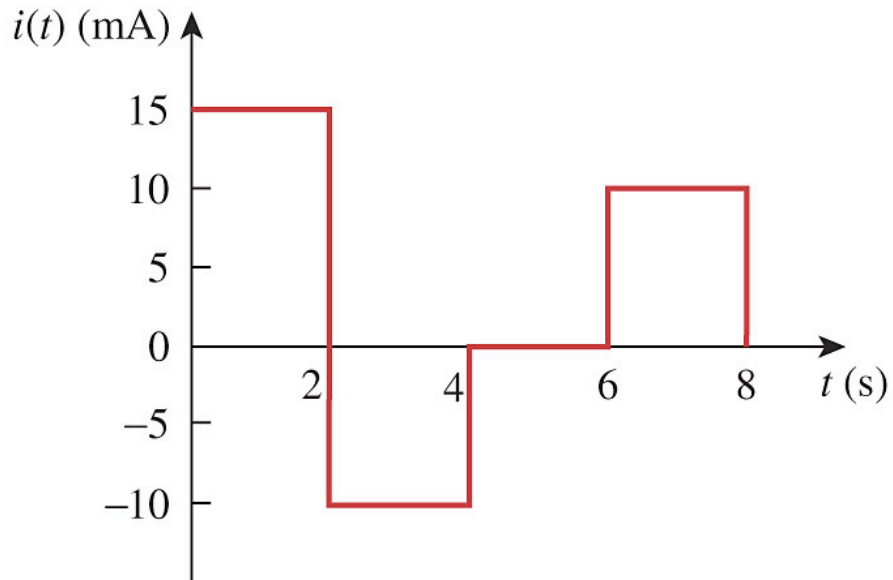


Problem 5

Find the voltage across the capacitors in the circuit below under dc conditions.

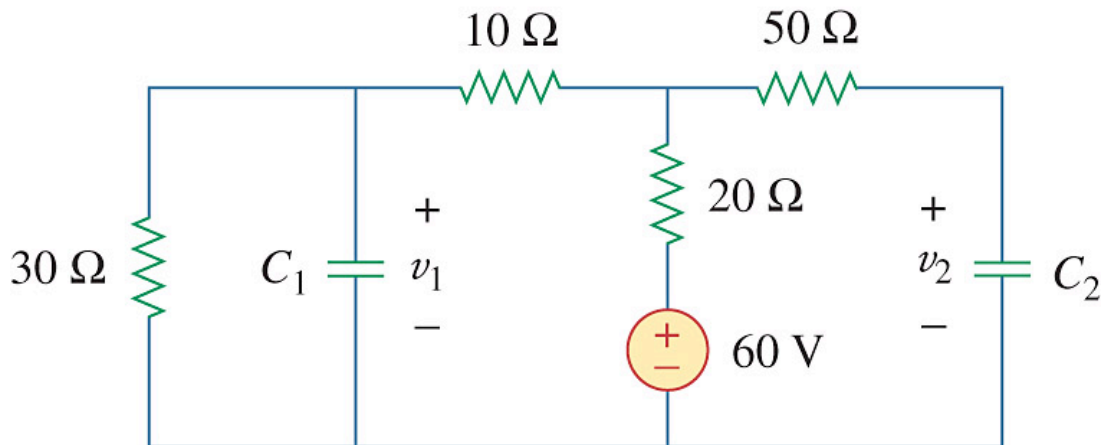


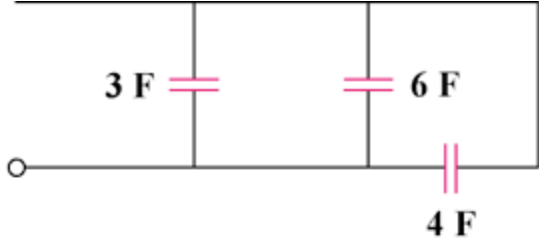Problem 6


Determine the equivalent capacitance for each of the circuits below



(a)

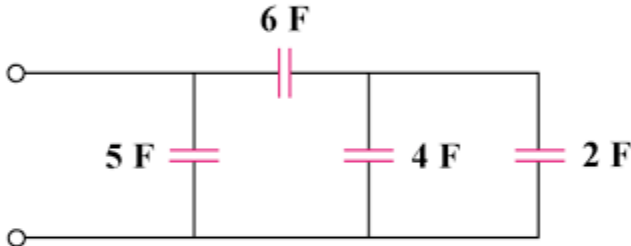

(b)

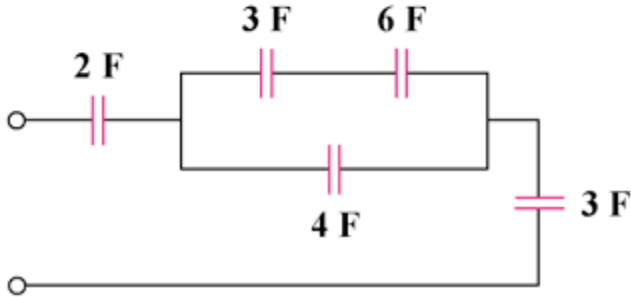


Problem 7

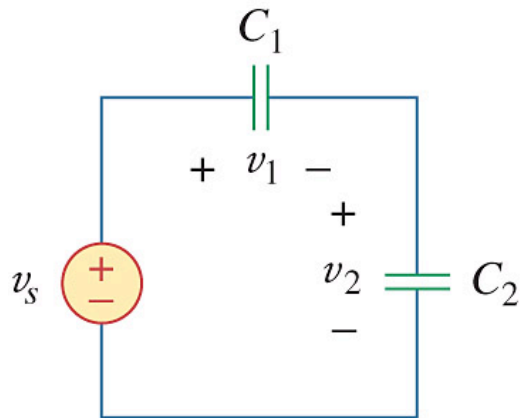
(a) Show that the voltage-division rule for two capacitors in series as shown is

$$v_1 = \frac{C_2}{C_1 + C_2} v_s, \quad v_2 = \frac{C_1}{C_1 + C_2} v_s$$

assuming that the initial conditions are zero.



(a)

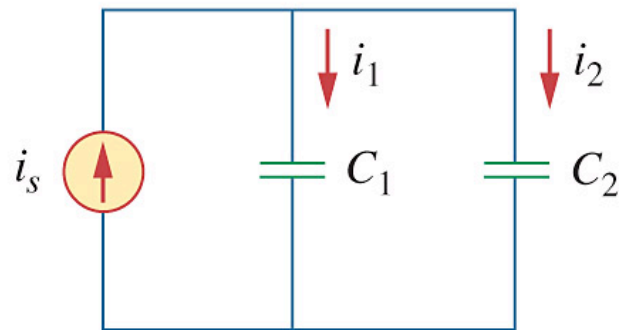

(b)

(b) For two capacitors in parallel as drawn, show that the current-division rule is

$$i_1 = \frac{C_1}{C_1 + C_2} i_s, \quad i_2 = \frac{C_2}{C_1 + C_2} i_s$$

assuming that the initial conditions are zero.