

Boise State University
Electrical Engineering Department

EE 210: Circuits I

Solution 1

(a) Before $t = 0$, $i = \frac{25}{3+2} = \underline{\mathbf{5\ A}}$

After $t = 0$, $i(t) = i(0)e^{-t/\tau}$

$$\tau = \frac{L}{R} = \frac{4}{2} = 2, \quad i(0) = 5$$

$$i(t) = \underline{\mathbf{5e^{-t/2} u(t)A}}$$

- (b) Before $t = 0$, the inductor acts as a short circuit so that the $2\ \Omega$ and $4\ \Omega$ resistors are short-circuited.

$$i(t) = \underline{\mathbf{6\ A}}$$


After $t = 0$, we have an RL circuit.

$$i(t) = i(0)e^{-t/\tau}, \quad \tau = \frac{L}{R} = \frac{3}{2}$$

$$i(t) = \underline{\mathbf{6e^{-2t/3} u(t)A}}$$

Solution 2

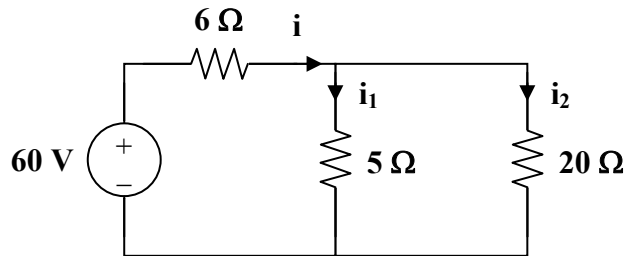At $t = 0^-$, the circuit has reached steady state so that the inductors act like short circuits.



$$i = \frac{60}{6 + 5 \parallel 20} = \frac{60}{10} = 6, \quad i_1 = \frac{20}{25} (6) = 4.8, \quad i_2 = 1.2$$
$$i_1(0) = 4.8 \text{ A}, \quad i_2(0) = 1.2 \text{ A}$$

For $t > 0$, the switch is closed so that the energies in L_1 and L_2 flow through the closed switch and become dissipated in the 5Ω and 20Ω resistors.

$$i_1(t) = i_1(0) e^{-t/\tau_1}, \quad \tau_1 = \frac{L_1}{R_1} = \frac{2.5}{5} = \frac{1}{2}$$

$$i_1(t) = \underline{4.8 e^{-2t} u(t) \text{ A}}$$

$$i_2(t) = i_2(0) e^{-t/\tau_2}, \quad \tau_2 = \frac{L_2}{R_2} = \frac{4}{20} = \frac{1}{5}$$

$$i_2(t) = \underline{1.2 e^{-5t} u(t) \text{ A}}$$