

Boise State University
Electrical Engineering Department

EE 210: Circuits I

Solution 1

For silicon, $\rho = 6.4 \times 10^2 \Omega\text{-m}$. $A = \pi r^2$. Hence,

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2} \longrightarrow r^2 = \frac{\rho L}{\pi R} = \frac{6.4 \times 10^2 \times 4 \times 10^{-2}}{\pi \times 240} = 0.033953$$

$$r = \underline{\underline{0.1843 \text{ m}}}$$

Solution 2

$$\text{At A, } 2 + 12 = i_1 \longrightarrow i_1 = \underline{\underline{14 \text{ A}}}$$

$$\text{At B, } 12 = i_2 + 14 \longrightarrow i_2 = \underline{\underline{-2 \text{ A}}}$$

$$\text{At C, } 14 = 4 + i_3 \longrightarrow i_3 = \underline{\underline{10 \text{ A}}}$$

Solution 3

$$-V_1 + 1 + 5 = 0 \longrightarrow V_1 = \underline{\underline{6 \text{ V}}}$$

$$-5 + 2 + V_2 = 0 \longrightarrow V_2 = \underline{\underline{3 \text{ V}}}$$

Solution 4

$$\text{For loop 1, } -12 + v + 2 = 0, \quad v = \underline{\underline{10 \text{ V}}}$$

$$\text{For loop 2, } -2 + 8 + 3i_x = 0, \quad i_x = \underline{\underline{-2 \text{ A}}}$$

Solution 5

Applying KVL around the entire outside loop we get,

$$-24 + v_1 + 10 + 12 = 0 \text{ or } v_1 = \underline{\underline{2 \text{ V}}}$$

Applying KVL around the loop containing v_2 , the 10-volt source, and the 12-volt source we get,

$$v_2 + 10 + 12 = 0 \text{ or } v_2 = \underline{\underline{-22 \text{ V}}}$$

Applying KVL around the loop containing v_3 and the 10-volt source we get,

$$-v_3 + 10 = 0 \text{ or } v_3 = \underline{10V}$$

Solution 6

Using voltage division,

$$V_o = \frac{4}{4+16}(16V) = \underline{6.4 V}$$

Solution 7

$$R_{eq} = 1 + 1/(1 + 1/2) = 1 + 1/(1 + 2/3) = 1 + 1/5/3 = \underline{1.625 \Omega}$$

Solution 8

$$R_{eq} = 3 + 2 // 4 // 1 = 3 + \frac{1}{1/2 + 1/4 + 1} = 3.5714$$


$$i_1 = \frac{40}{3.5714} = \underline{11.2 A}$$

$$v_1 = 0.5714x i_1 = 6.4V, \quad i_2 = \frac{v_1}{4} = \underline{1.6 A}$$

$$i_4 = v_1/1 = \underline{6.4 A}, \quad i_5 = v_1/2 = \underline{3.2 A}, \quad i_3 = i_4 + i_5 = \underline{9.6 A}.$$

Solution 9

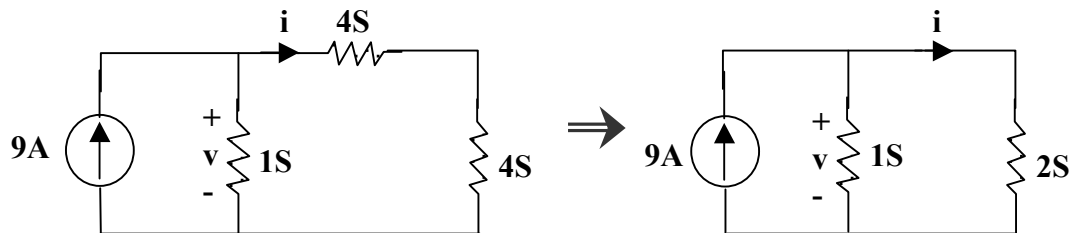Combining the conductance leads to the equivalent circuit below



$$6S // 3S = \frac{6 \times 3}{9} = 2S \text{ and } 2S + 2S = 4S$$

Using current division,

$$i = \frac{1}{1 + \frac{1}{2}}(9) = \underline{6 \text{ A}}, v = 3(1) = \underline{3 \text{ V}}$$

Solution 10

Applying KVL,

$$-20 + 10 + 10I - 30 = 0, \quad I = 4$$

$$10 = RI \quad \longrightarrow \quad R = \frac{10}{I} = \underline{2.5 \Omega}$$