

**Boise State University**  
**Electrical Engineering Department**

EE 210: Circuits I

---

**Solution 1**

For mesh 1,

$$-10 - 2I_x + 10I_1 - 6I_2 = 0$$

But  $I_x = I_1 - I_2$ . Hence,

$$10 = -2I_1 + 2I_2 + 10I_1 - 6I_2 \quad \longrightarrow \quad 5 = 4I_1 - 2I_2 \quad (1)$$

For mesh 2,

$$12 + 8I_2 - 6I_1 = 0 \quad \longrightarrow \quad 6 = 3I_1 - 4I_2 \quad (2)$$

Solving (1) and (2) leads to

$$\underline{I_1 = 0.8 \text{ A}, I_2 = -0.9 \text{ A}}$$

**Solution 2**

Assume R is in kilo-ohms.



$$V_2 = 4\text{k}\Omega \times 18\text{mA} = \underline{72\text{V}}, \quad V_1 = 100 - V_2 = 100 - 72 = \underline{28\text{V}}$$

Current through R is

$$i_R = \frac{3}{3+R} i_o, \quad V_1 = i_R R \quad \longrightarrow \quad 28 = \frac{3}{3+R} (18)R$$

$$\text{This leads to } R = 84/26 = \underline{\underline{3.23 \text{ k}\Omega}}$$

### Solution 3

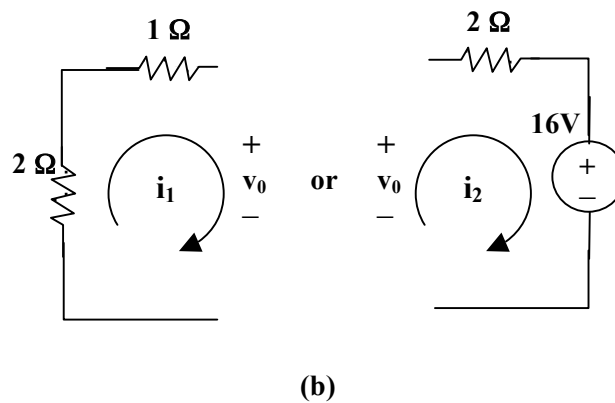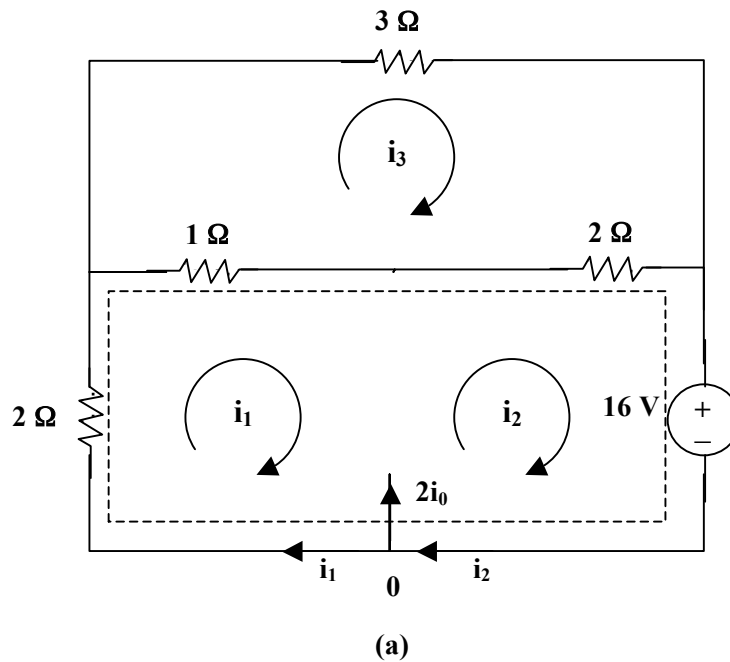

For the supermesh in figure (a),

$$3i_1 + 2i_2 - 3i_3 + 16 = 0 \quad (1)$$


$$\text{At node 0, } i_2 - i_1 = 2i_0 \text{ and } i_0 = -i_1 \text{ which leads to } i_2 = -i_1 \quad (2)$$

$$\text{For loop 3, } -i_1 - 2i_2 + 6i_3 = 0 \text{ which leads to } 6i_3 = -i_1 \quad (3)$$

Solving (1) to (3),  $i_1 = (-32/3)\text{A}$ ,  $i_2 = (32/3)\text{A}$ ,  $i_3 = (16/9)\text{A}$

$i_0 = -i_1 = \underline{10.667 \text{ A}}$ , from fig. (b),  $v_0 = i_3 - 3i_1 = (16/9) + 32 = \underline{33.78 \text{ V}}$ .

**Solution 4**

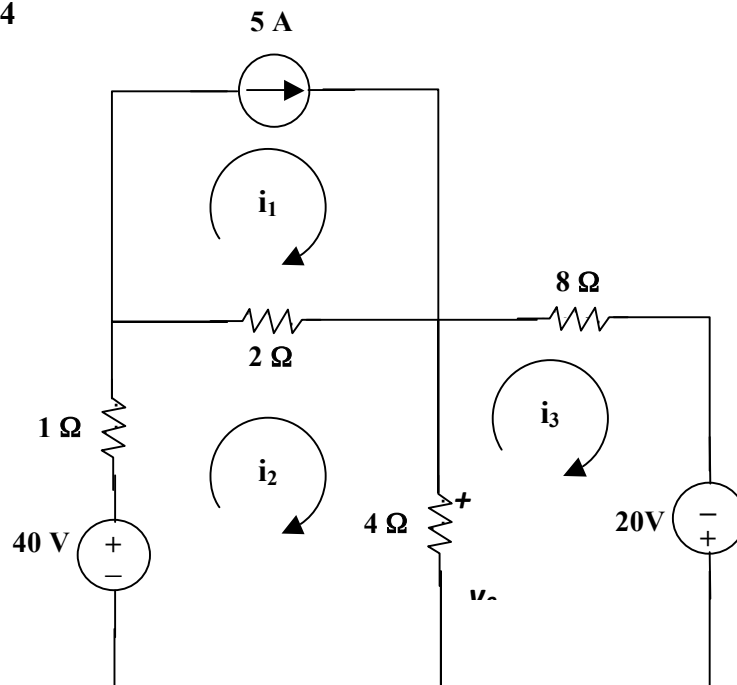

For loop 1,  $i_1 = 5\text{A}$  (1)


For loop 2,  $-40 + 7i_2 - 2i_1 - 4i_3 = 0$  which leads to  $50 = 7i_2 - 4i_3$  (2)

For loop 3,  $-20 + 12i_3 - 4i_2 = 0$  which leads to  $5 = -i_2 + 3i_3$  (3)

Solving with (2) and (3),  $i_2 = 10\text{ A}$ ,  $i_3 = 5\text{ A}$

And,  $v_0 = 4(i_2 - i_3) = 4(10 - 5) = \underline{20\text{ V}}$ .

### Solution 5

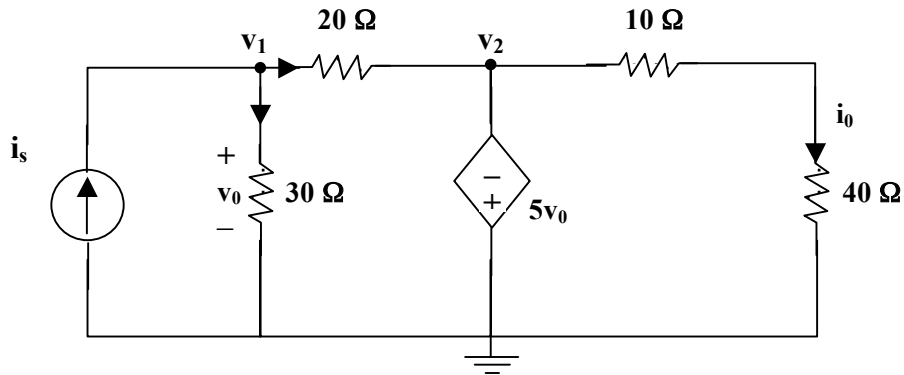

At node 1,  $i_s = (v_1/30) + ((v_1 - v_2)/20)$  which leads to  $60i_s = 5v_1 - 3v_2$  (1)

But  $v_2 = -5v_0$  and  $v_0 = v_1$  which leads to  $v_2 = -5v_1$

Hence,  $60i_s = 5v_1 + 15v_1 = 20v_1$  which leads to  $v_1 = 3i_s$ ,  $v_2 = -15i_s$

$i_0 = v_2/50 = -15i_s/50$  which leads to  $i_0/i_s = -15/50 = \underline{\underline{-0.3}}$