

Boise State University
Electrical Engineering Department

EE 210: Circuits I

Solution 1

Let the voltage at the input of the op amp be v_a .

$$v_o = 1 \text{ V}, \quad \frac{3-v_a}{4k} = \frac{v_a-v_o}{10k} \quad \longrightarrow \quad \frac{3-1}{4} = \frac{1-v_o}{10}$$

$$v_o = \underline{\underline{-4 \text{ V}}}.$$

Solution 2

At the inverting terminal, $v=0$ so that KCL gives

$$\frac{v_s - 0}{R_1} = \frac{0}{R_2} + \frac{0 - v_o}{R_f} \quad \longrightarrow \quad \frac{v_o}{v_s} = -\frac{R_f}{R_1}$$

Solution 3

$$v_o = -\left[\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right]$$

$$= -\left[\frac{30}{10}(1) + \frac{30}{20}(2) + \frac{30}{30}(-3) \right]$$

$$v_o = \underline{\underline{-3 \text{ V}}}$$

Solution 4

This is a summing amplifier.

$$v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right) = -\left(\frac{50}{10}(2) + \frac{50}{20} v_2 + \frac{50}{50}(-1) \right) = -9 - 2.5v_2$$

Thus,

$$v_o = -16.5 = -9 - 2.5v_2 \quad \longrightarrow \quad \underline{\underline{v_2 = 3 \text{ V}}}$$

Solution 5

Using eq. (5.18), $R_1 = 2k\Omega$, $R_2 = 30k\Omega$, $R_3 = 2k\Omega$, $R_4 = 20k\Omega$

$$v_o = \frac{30(1+2/30)}{2(1+2/20)}v_2 - \frac{30}{2}v_1 = \frac{32}{2.2}(2) - 15(1) = \underline{14.09 \text{ V}}$$