

Boise State University
Electrical Engineering Department

EE 210: Circuits I



Solution 1


(a) Let v_a and v_b be respectively the voltages at the inverting and noninverting terminals of the op amp

$$v_a = v_b = 4V$$

At the inverting terminal,

$$1\text{mA} = \frac{4 - v_o}{2\text{k}} \longrightarrow v_o = 2V$$

(b)

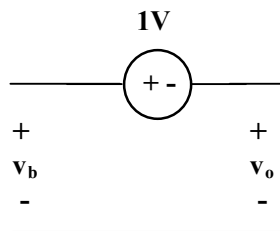

Since $v_a = v_b = 3V$,

$$-v_b + 1 + v_o = 0 \longrightarrow v_o = v_b - 1 = 2V$$

Solution 2

(a) Let v_1 be the voltage at the node where the three resistors meet. Applying KCL at this node gives

$$i_s = \frac{v_1}{R_2} + \frac{v_1 - v_o}{R_3} = v_1 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{v_o}{R_3} \quad (1)$$

At the inverting terminal,

$$i_s = \frac{0 - v_1}{R_1} \quad \longrightarrow \quad v_1 = -i_s R_1 \quad (2)$$

Combining (1) and (2) leads to

$$i_s \left(1 + \frac{R_1}{R_2} + \frac{R_1}{R_3} \right) = -\frac{v_o}{R_3} \quad \longrightarrow \quad \frac{v_o}{i_s} = - \left(R_1 + R_3 + \frac{R_1 R_3}{R_2} \right)$$

(b) For this case,


$$\frac{v_o}{i_s} = - \left(20 + 40 + \frac{20 \times 40}{25} \right) \text{k}\Omega = \underline{-92 \text{k}\Omega}$$

$$= \underline{-92 \text{k}\Omega}$$

Solution 3

We convert the current source and back to a voltage source.

$$2 \parallel 4 = \frac{4}{3}$$

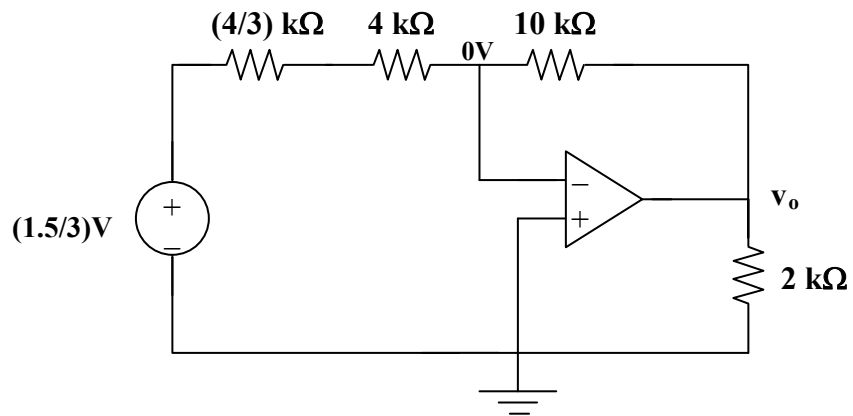


$$v_o = -\frac{10\text{k}}{\left(4 + \frac{4}{3}\right)\text{k}} \left(\frac{1.5}{3}\right) = -937.5 \text{ mV.}$$

$$i_o = \frac{v_o}{2\text{k}} + \frac{v_o - 0}{10\text{k}} = -562.5 \text{ } \mu\text{A.}$$

Solution 4

Determine V_o in terms of V_1 and V_2 .

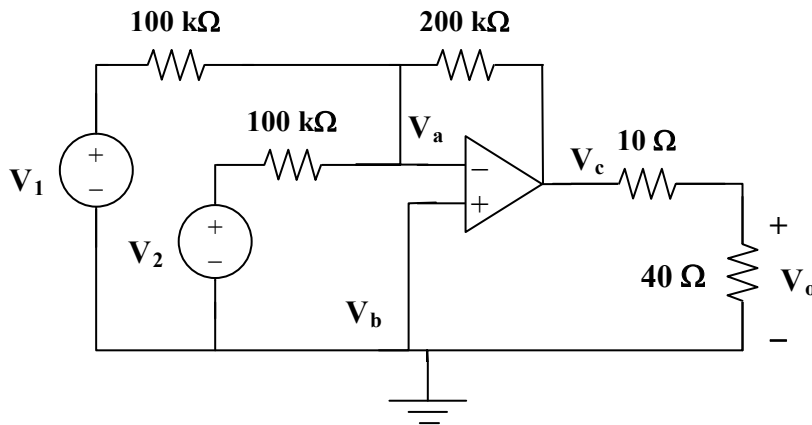

Step 1. Label the reference and node voltages in the circuit, see above. Note we now can consider nodes a and b, we cannot write a node equation at c without introducing another unknown. The node equation at a is $[(V_a - V_1)/10^5] + [(V_a - V_2)/10^5] + 0 + [(V_a - V_c)/2 \times 10^5] = 0$. At b it is clear that $V_b = 0$. Since we have two equations and three unknowns, we need another equation. We do get that from the constraint equation, $V_a = V_b$. After we find V_c in terms of V_1 and V_2 , we then can determine V_o which is equal to $[(V_c - 0)/50]$ times 40.

Step 2. Letting $V_a = V_b = 0$, the first equation can be simplified to,

$$[-V_1/10^5] + [-V_2/10^5] + [-V_c/2 \times 10^5] = 0$$

Taking V_c to the other side of the equation and multiplying everything by 2×10^5 , we get,

$$V_c = -2V_1 - 2V_2$$

Now we can find V_o which is equal to $(40/50)V_c = 0.8[-2V_1 - 2V_2]$

$$V_o = -1.6V_1 - 1.6V_2.$$