
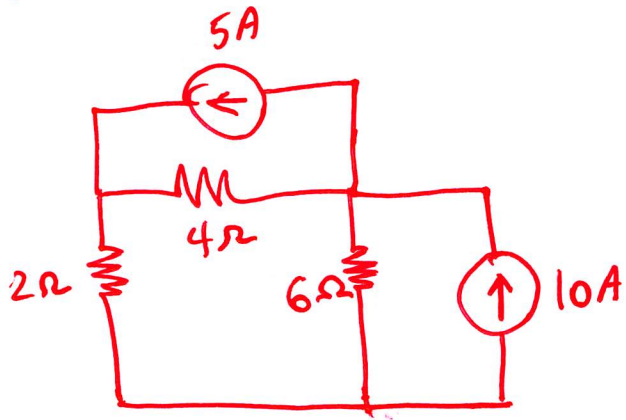


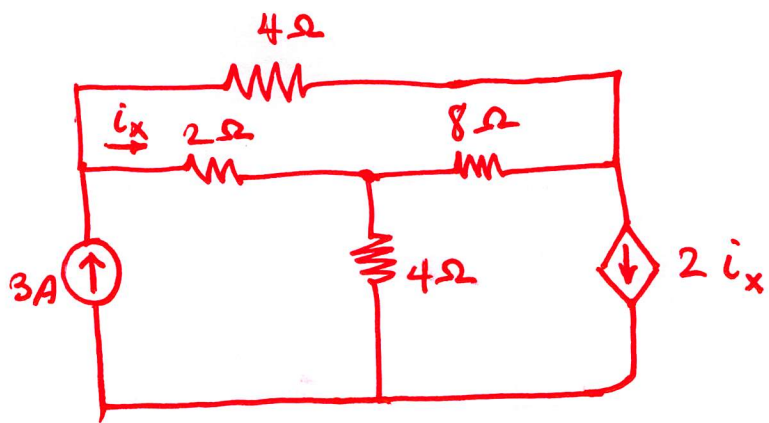
1) Calculate the node voltages in the circuit shown



2) Det. the voltages @ the nodes



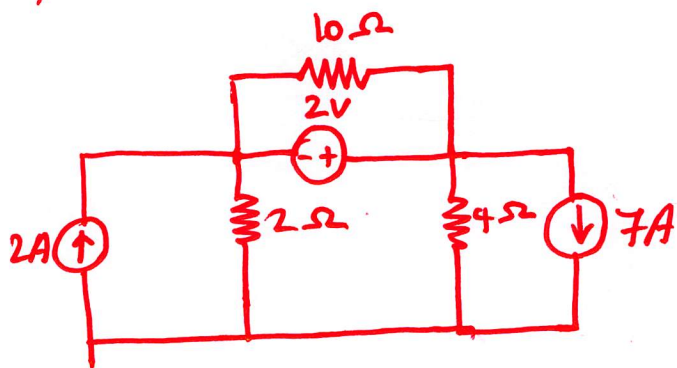3) For the circuit below find the node voltages



4) Find the node voltages in the circuit below:

