
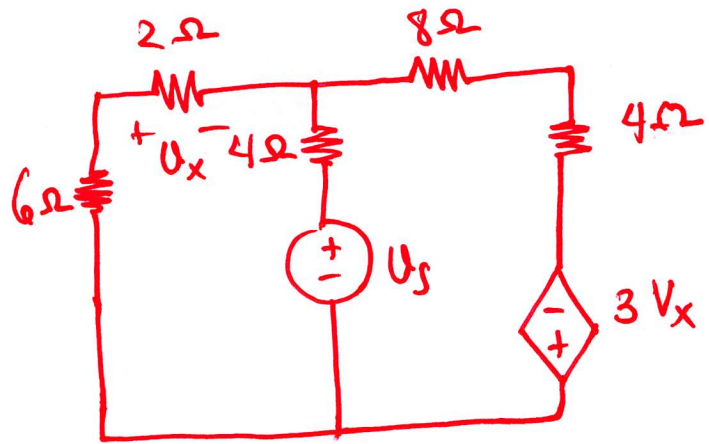


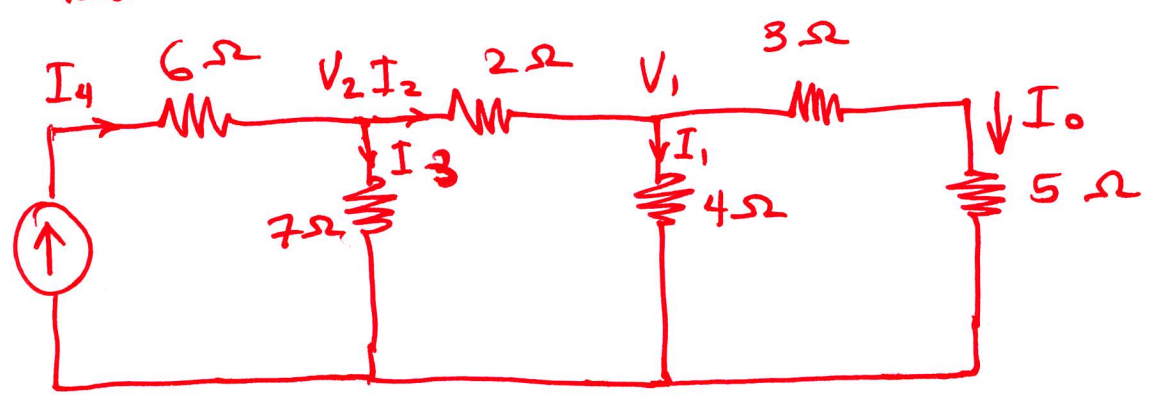
1) For the circuit shown find I_o when $U_s = 12V$ and $U_s = 24V$




2) Assume $I_0 = 1A$ and use linearity to find I_0 's actual value.



Problem 3) Find U using superposition

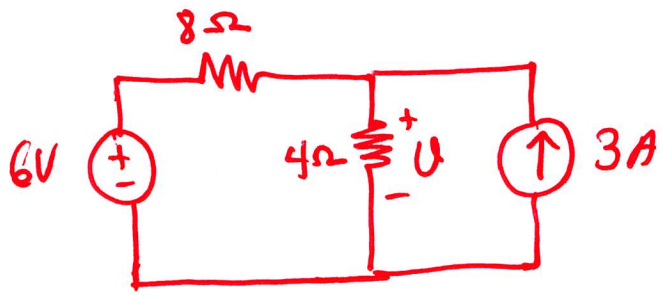

4) Find i_o using Superposition.

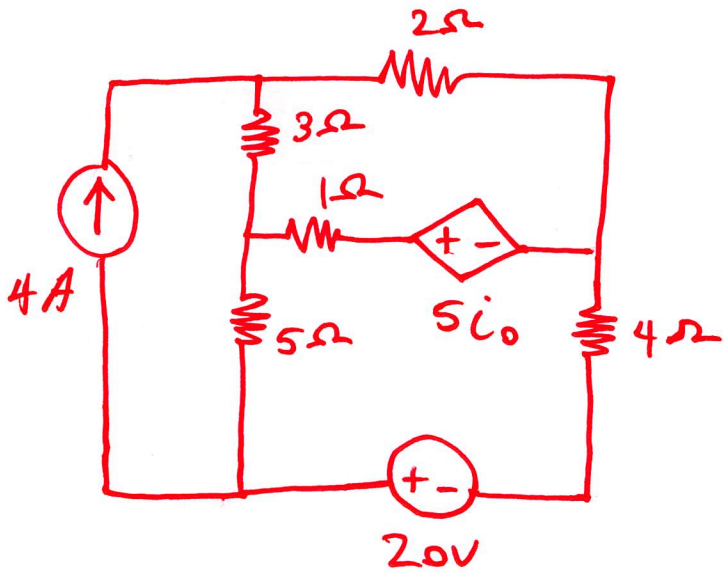

5) Find i using Superposition

