

Electric Circuits

Hani Mehrpouyan,

Department of Electrical and Computer Engineering,
Boise State University
Lecture 12 (First Order Circuits)
Nov 2nd, 2015

Overview


- This chapter examines RC and LC circuits' reaction to switched sources.
- The circuits are referred to as first order circuits.
- Three special functions, the unit step, unit impulse, and unit ramp function are also introduced.
- Both source free and switched sources are examined.

First Order Circuits

- A first order circuit is characterized by a first order differential equation.
- There are two types of first order circuits:
 - Resistive capacitive, called RC
 - Resistive inductive, called RL
- There are also two ways to excite the circuits:
 - Initial conditions
 - Independent sources


Source Free RC Circuit

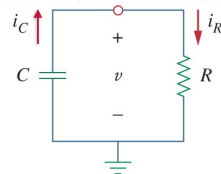- A source free RC circuit occurs when its dc source is suddenly disconnected.
- The energy stored in the capacitor is released to the resistors.
- Consider a series combination of a resistor and a initially charged capacitor as shown:



Natural Response

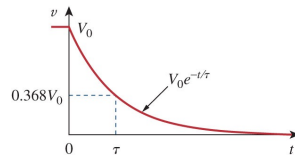- The result shows that the voltage response of the RC circuit is an exponential decay of the initial voltage.
- Since this is the response of the circuit without any external applied voltage or current, the response is called the natural response.




Time Constant

- The speed at which the voltage decays can be characterized by how long it takes the voltage to drop to $1/e$ of the initial voltage.
- This is called the time constant and is represented by τ .
- By selecting $1/e$ as the reference voltage:
$$\tau = RC$$
- The voltage can thus be expressed as:

$$v(t) = V_0 e^{-t/\tau}$$

Time Constant II

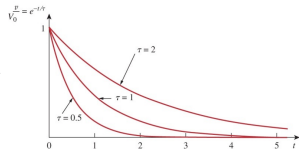- After five time constants the voltage on the capacitor is less than one percent.
- After five time constants a capacitor is considered to be either fully discharged or charged
- A circuit with a small time constant has a fast response and vice versa.



RC Discharge

- With the voltage known, we can find the current:

$$i_R(t) = \frac{V_0}{R} e^{-t/\tau}$$

- The power dissipated in the resistor is:

$$p(t) = \frac{V_0^2}{R} e^{-2t/\tau}$$

- The energy absorbed by the resistor is:

$$w_R(t) = \frac{1}{2} C V_0^2 (1 - e^{-2t/\tau})$$

Solved Problem
