





## Source Free RL Circuit

- After integration:

$$i(t) = I_0 e^{-Rt/L}$$

- Once again, the natural response is an exponentially decaying current.
- The time constant in this case is:

$$\tau = \frac{L}{R}$$

- The same principles as the RC circuit apply here.

Solved Problem

