

Resistivity of Common Materials

TABLE 2.1

Resistivities of common materials.


Material	Resistivity ($\Omega\cdot\text{m}$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Aluminum	2.8×10^{-8}	Conductor
Gold	2.45×10^{-8}	Conductor
Carbon	4×10^{-5}	Semiconductor
Germanium	47×10^{-2}	Semiconductor
Silicon	6.4×10^2	Semiconductor
Paper	10^{10}	Insulator
Mica	5×10^{11}	Insulator
Glass	10^{12}	Insulator
Teflon	3×10^{12}	Insulator

Short and Open Circuits

- A connection with almost zero resistance is called a short circuit.
- Ideally, any current may flow through the short.
- In practice this is a connecting wire.
- A connection with infinite resistance is called an open circuit.
- Here, no matter the voltage, no current flows.

Linearity

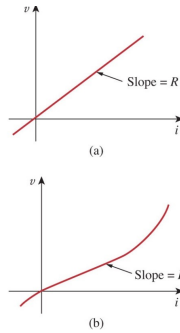- Not all materials obey Ohm's Law.
- Resistors that do are called linear resistors because their current voltage relationship is always linearly proportional.
- Diodes and light bulbs are examples of non-linear elements.



Power Dissipation

- Running current through a resistor dissipates power.

$$p = vi = i^2 R = \frac{v^2}{R}$$


- The power dissipated is a non-linear function of current or voltage
- Power dissipated is always positive
- A resistor can never generate power



Solved Problem




Solved Problem

Boise State University 

Solved Problem

Hani Mehrpouyan (hani.mehr@ieee.org) Boise State ©2017 11

Boise State University 

Solved Problem

Hani Mehrpouyan (hani.mehr@ieee.org) Boise State ©2017 12

Solved Problem
